

## APPLICATIONS

### SINGLE POLE SWITCHES

- used when only one conductor is to be switched
- lighting in a room where lamp is controlled from one location
- switching of 120V Fractional Horse Power motors

### DOUBLE POLE SWITCHES

- used when two conductors are switched at the same time
- available in many current and voltage ratings
- often used for 240V heaters and appliances and single phase 240V motors

### THREE POLE SWITCH

- used when 3 conductors need to be switched simultaneously
- found mostly in 3 phase circuits

### THREE WAY SWITCH

- used to control load from more than one location
- often used in corridor lighting

### FOUR WAY SWITCH


- used with 3 way switch to control load from more than 2 locations
- can be used as a 3 way switch if configured right

## DIAGRAMS

### Schematic Diagrams

- shows logical sequence of operation of a circuit without regard to physical location of components
- very useful when troubleshooting
- also called elementary or ladder diagrams

### LADDER DIAGRAM

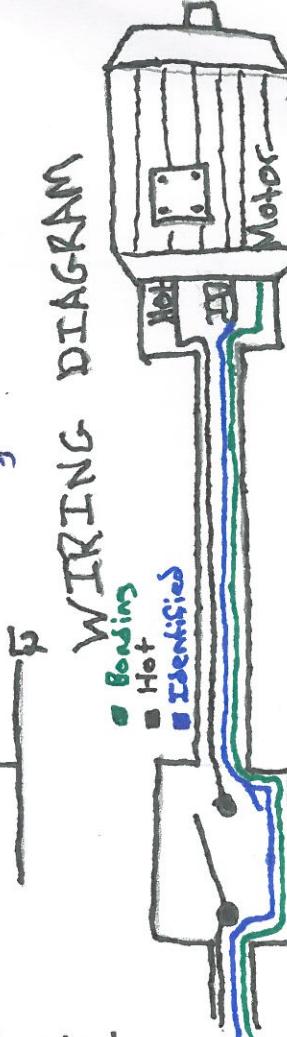

## SWITCHING CIRCUITS

*Symbols*

Single Pole  
Single Throw




Single Pole  
Double Throw




Double Pole  
Single Throw




3 Position

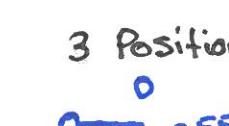


3 Position Selector

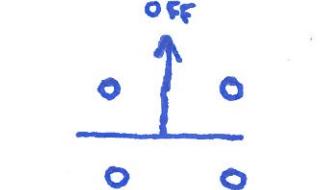


Double NO Push button

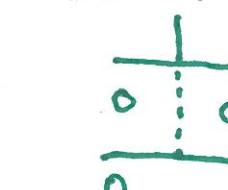

Rotary Type

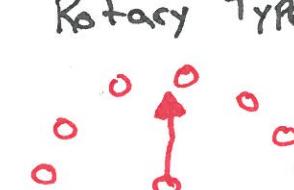

Resistor

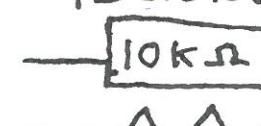

3 Pole



Double Throw



or



Double Throw



Normally Open Push button



(NO)

Double NC Push button



Battery



Ground



3 Way



4 Way



Normally Closed Pushbutton



(NC)

Sliding Type



Lamp



Transformer

